

## SOLUTIONS OF TUT SHEET NO. 6

Q1 (Ans):

*Solution* From Eq. (11.29),

$$f_{\beta} = \frac{1}{2\pi r_{b'e}(C_c + C_e)} = \frac{1}{2\pi(1\text{ K})(1.2\text{ pF})} = 133\text{ MHz}$$

And from Eq. (11.30),

$$f_T = \frac{g_m}{2\pi(C_c + C_e)} = \frac{50\text{ mA/V}}{2\pi(1.2\text{ pF})} = 6.6\text{ GHz}$$

$f_T$  represents the highest frequency at which a transistor will provide a gain. The above numbers show that modern bipolar transistors can provide gains up to frequencies in the GHz range.

Q2(Ans):

**Solution. (i)**  $V_T = \frac{kT}{q} = \frac{T}{11,600}$

Hence  $g_m = \frac{|I_C|}{V_T} = \frac{10 \times 10^{-3} \times 11,600}{300} = 0.3866\text{ S}$

(ii),  $r_{b'e} = \frac{h_{fe}}{g_m} = \frac{100}{0.3866} = 258.6\ \Omega$

(iii)  $r_{bb}' = h_{ie} - r_{b'e} = 500 - 258.6 = 241.4\ \Omega$

(iv)  $r_{b'c} = \frac{r_{b'e}}{h_{re}} = \frac{258.6}{10^{-4}} = 258.4 \times 10^4\ \Omega$

(v)  $g_{ce} = h_{oe} - (1 + h_{fe})g_{bc} = 2 \times 10^{-4} - (1 + 100) \times \frac{1}{258.6 \times 10^4} = S = 1.61 \times 10^{-4}\text{ S}$

(vi)  $C_e = \frac{g_m}{2\pi f_T} = \frac{0.3866}{2\pi \times 50 \times 10^6}\text{ F} = 1.235 \times 10^{-9}\text{ F}$

(vii)  $C_c = C_{ob} = 3\text{ pF.}$

Q3(Ans):

**Solution. (i)** 
$$g_m = \frac{|I_C|}{V_T} = \frac{8 \times 10^{-3} \times 11600}{300} = 0.309 \text{ S}$$

$$r_{b'e} = \frac{h_{fe}}{g_m} = \frac{100}{0.309} \Omega = 323 \Omega$$

(ii) 
$$r_{bb'} = h_{ie} - r_{b'e} = 800 - 323 = 477 \Omega$$

(iii) 
$$|A_{IS}| = \frac{h_{fe}}{\sqrt{1 + (f/f_\beta)^2}}$$

Substituting the values, 
$$14 = \frac{100}{\sqrt{1 + (8/f_\beta)^2}}$$
 where  $f_\beta$  is in MHz

$$1 + \left(\frac{8}{f_\beta}\right)^2 = \left(\frac{100}{14}\right)^2 = 51.02$$

Hence 
$$f_\beta = \frac{8}{\sqrt{50.02}} = 1.311 \text{ MHz}$$

(iv) 
$$f_T = h_{fe} \cdot f_\beta = 100 \times 1.311 = 131.1 \text{ MHz}$$

(v) But 
$$f_T = \frac{g_m}{2\pi(C_c + C_e)}$$

Hence 
$$C_c + C_e = \frac{g_m}{2\pi f_T} = \frac{0.309}{2\pi \times 131.1 \times 10^6} \text{ F} = 375 \text{ pF}$$

$$C_c = 4 \text{ pF}$$

Hence 
$$C_e = (375 - 4) = 371 \text{ pF.}$$

Q4(Ans):

**Solution.**

$$I_C \approx I_E = 4 \text{ mA.}$$

$$g_m = \frac{|I_C|}{V_T} = \frac{4 \times 10^{-3} \times 11600}{300} = 0.155 \text{ S}$$

Diffusion constant for holes  $D_B = 50 \text{ cm}^2/\text{sec.}$

Base width

$$W = 2.5 \times 10^{-4} \text{ cm.}$$

Hence

$$C_{De} = g_m \cdot \frac{W^2}{2 D_B} = \frac{0.155 \times (2.5 \times 10^{-4})^2}{2 \times 50} \text{ F} = 96.9 \text{ pF}$$

For  $J_E$  forward biased,

$$C_e = C_{De} + C_{Te} \approx C_{De}$$

But

$$C_e = \frac{g_m}{2\pi f_T}$$

Hence

$$f_T = \frac{g_m}{2\pi C_e} = \frac{0.155}{2\pi \times 96.9 \times 10^{-12}} \text{ Hz} = 254 \text{ MHz.}$$

Q5 & Q6 (Ans):

**Rise Time** The response of the low-pass circuit of Fig. 12.2 to a step input of amplitude  $V$  is exponential with a time constant  $R_2C_2$ . Since the capacitor voltage cannot change instantaneously, the output starts from zero and rises toward the steady-state value  $V$ , as shown in Fig. 12.8. The output is given by

$$v_o = V(1 - e^{-t/R_2C_2}) \quad (12.19)$$

The time required for  $v_o$  to reach one-tenth of its final value is readily found to be  $0.1R_2C_2$ , and the time to reach nine-tenths its final value is  $2.3R_2C_2$ . The difference between these two values is called the *rise time*  $t_r$  of the circuit and is shown in Fig. 12.8. The time  $t_r$  is an indication of how fast the amplifier can respond to a discontinuity in the input voltage. We have, using Eq. (12.7),

$$t_r = 2.2R_2C_2 = \frac{2.2}{2\pi f_H} = \frac{0.35}{f_H} \quad (12.20)$$

Note that the rise time is inversely proportional to the upper 3-dB frequency. For an amplifier with 1 MHz bandwidth,  $t_r = 0.35 \mu\text{s}$ .

Consider a pulse of width  $t_p$ . What must be the high 3-dB frequency  $f_H$  of an amplifier used to amplify this signal without excessive distortion? A reasonable answer to this question is: Choose  $f_H$  equal to the reciprocal of the pulse width,  $f_H = 1/t_p$ . From Eq. (12.20) we then have  $t_r = 0.35t_p$ . Using this relationship, the (shaded) pulse in Fig. 12.9 becomes distorted into the (solid) waveform, which is clearly recognized as a pulse.

**Tilt or Sag** If a step of amplitude  $V$  is impressed on the high-pass circuit of Fig. 12.1, the output is

$$v_o = Ve^{-t/R_1C_1} \quad (12.21)$$

For times  $t$  which are small compared with the time constant  $R_1C_1$ , the response is given by

$$v_o \approx V\left(1 - \frac{t}{R_1C_1}\right) \quad (12.22)$$

From Fig. 12.10 we see that the output is tilted, and the percent tilt, or sag, in time  $t_1$  is given by

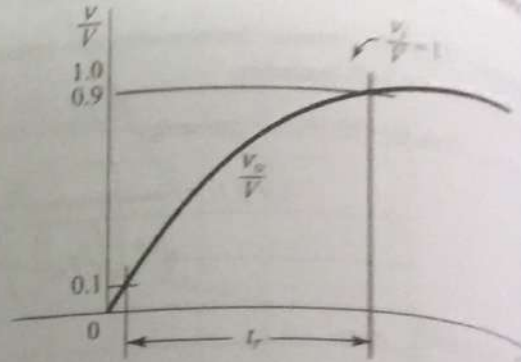


Fig. 12.8 Step-voltage response of the low-pass RC circuit. The rise time  $t_r$  is indicated.

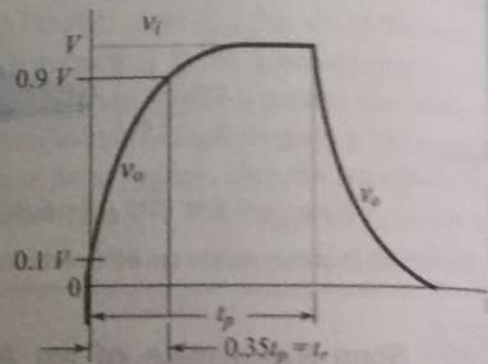


Fig. 12.9 Pulse response for the case  $f_H = 1/t_p$ .

$$P \equiv \frac{V - V'}{V} \times 100 = \frac{t_1}{R_1 C_1} \times 100\% \quad (12.23)$$

It is found<sup>6</sup> that this same expression is valid for the tilt of each half cycle of a symmetrical square wave of peak-to-peak value  $V$  and period  $T$  provided that we set  $t_1 = T/2$ . If  $f = 1/T$  is the frequency of the square wave, then, using Eq. (12.3), we may express  $P$  in the form

$$P = \frac{T}{2R_1 C_1} \times 100 = \frac{1}{2fR_1 C_1} \times 100 = \frac{\pi f_L}{f} \times 100\% \quad (12.24)$$

Note that the tilt is directly proportional to the lower 3-dB frequency. If we wish to pass a 50-Hz square wave with less than 10 percent sag, then  $f_L$  must not exceed 1.6 Hz.

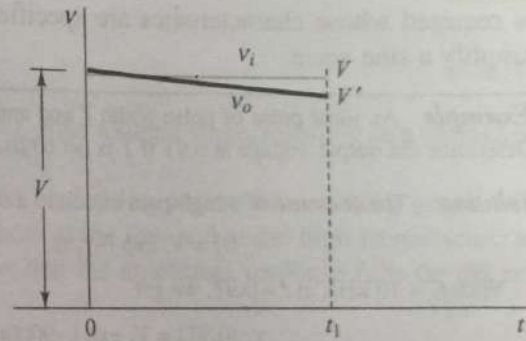


Fig. 12.10 The response  $v_o$ , when a step  $v_i$ , is applied to a high-pass RC circuit, exhibits a tilt.